
Table of Contents

Part 1: Fundamentals

Chapter 1: History	9
The People	9
1.1: Hans Christian Ørsted	9
1.2: Michael Faraday	9
1.3: Heinrich Wilhelm Dove	9
1.4: David Hughes	10
1.5: Alexander Graham Bell	10
1.6: Other Early Inventors	12
1.7: Gerhard Fisher	13
1.8: Later Contributors	13
The Applications	14
1.9: Military Use	14
1.10: Commercial & Industrial Use	15
1.11: Treasure Hunting	16
The Technologies	17
1.12: BFO	17
1.13: IB	17
1.14: PI	18
The Companies	18
1.15: Fisher	18
1.16: White's	19
1.17: Garrett	20
1.18: Bounty Hunter	21
1.19: Compass	21
1.20: Teknetics	22
1.21: C&G/Tesoro	22
1.22: Minelab	23
1.23: XP	23
1.24: Nokta	24
1.25: Others	24
Chapter 2: Types of Detectors	27
Proximity Effect	27
2.1: BFO	27
2.2: Energy Theft	28
2.3: Off-Resonance	28
2.4: PLL	29
Induction Balance	29

2.5: IB	29
2.6: TR	29
2.7: RF	30
2.8: VLF	30
2.9: VLF/TR	31
2.10: Multifrequency	31
Pulse Induction	32
2.11: Basic PI	32
2.12: Ground Balance PI	32
2.13: Other PI Developments	33
Other Jargon	33
2.14: Continuous-Time vs Discrete-Time: Transmitters	33
2.15: Continuous-Time vs Discrete-Time: Demodulators	34
2.16: Continuous-Time vs Discrete-Time: Signal Processing	36
2.17: Frequency Domain vs Time Domain	36
2.18: Synchronous Demodulation	36
2.19: Direct Sampling	37
2.20: Hybrid Designs	38
2.21: The Future	38
Chapter 3: Magnetics & Induction	39
Magnetics	39
3.1: Static Magnetic Fields	39
3.2: Alternating Magnetic Fields	41
3.3: Coil Fields	43
Induction	46
3.4: Induction Balance	47
Explore	49
3.5: Compass Experiments	49
3.6: Visualizing Magnetic Fields	50
Chapter 4: Target Responses	51
Magnetic Responses	51
4.1: Magnetic Lag	51
4.2: Ground vs Iron	54
4.3: Hot Rocks	55
4.4: Viscous Magnetic Response	56
4.5: Earth Field	56
Eddy Responses	56
4.6: The Physics of Eddy Currents	59
4.7: Eddy Depth Distribution	61
4.8: Skin Effect	62
4.9: Eddy Surface Distribution	63
4.10: Target Field Phase	65
4.11: Target Field Amplitude	66
4.12: RL Target Model	67
4.13: Wire Loop Tau	68
4.14: Salt Water	70
Transmitter Effects	71
Explore	72
4.15: Alloy Conductivities	72
4.16: Practical Test Targets	73
4.17: Measuring Target Taus	75

4.18: Fun With Eddy Currents	77
Chapter 5: Complex Responses	79
Problem Targets	79
5.1: Composite Responses — Iron	79
5.2: Positional Quirks	82
5.3: Composite Responses — Co-Located Targets	83
5.4: Adjacent Targets	84
5.5: Difficult Metals	85
5.6: Composite Responses — Multiple Domain Targets	85
5.7: Size & Shape Effects	86
Time Domain Responses	88
5.8: Ramp Response	88
5.9: Step Response	91
5.10: Exponential Response	93
Explore	94
5.11: Testing Recovery Speed	94
5.12: The Monte Nail Board	94
5.13: Simple Test Jig	95
5.14: Gold versus Aluminum	96

Part 2: Coils

Chapter 6: Coil Types	99
Planar Coils	99
6.1: Mono Coil	99
6.2: Double-O Coil	100
6.3: Double-D Coil	101
6.4: Other Overlaps	102
6.5: Concentric Coil	102
6.6: Omega Coil	103
6.7: Figure-8 Coil	104
6.8: Butterfly Coil	105
Non-Planar Coils	106
6.9: Coaxial Coil	106
6.10: Orthogonal Coil	107
Dual Coils	109
Explore	110
6.11: Coil Sizes & Weights	110
Chapter 7: Coil Performance	113
Transmit	113
7.1: Using the Probe	113
7.2: Comparative Measurements	115
Receive	116
7.3: Receive Coil Physics	116
7.4: Detection Patterns	117
7.5: Concentric Coils	120
7.6: Overlapped Coils	122
7.7: Coaxial Coils	124
7.8: Figure-8 Coils	124
Other Considerations	124
7.9: Mineralization & Lift-Off	124
7.10: Target Separation	127

7.11: EMI	128
7.12: Spacial Alignment	128
Explore	129
7.13: More Power	129
7.14: The Math of Depth: Part 1	129
7.15: The Math of Depth: Part 2	130
7.16: RX Coil Size Revisited	131
Chapter 8: Building Coils	133
8.1: Coil Windings	133
8.1.1: Coil Parametrics	133
8.1.2: Wire	135
8.1.3: Coil Windings	137
8.1.4: Winding Coils	139
8.1.5: Bondable Wire	140
8.1.6: Automated Winder	140
8.2: Other Elements	141
8.2.1: Coil Shell	141
8.2.2: Potato Chipping	142
8.2.3: Cable	142
8.2.4: Connector	143
8.2.5: Shielding	144
8.2.6: Stabilization	147
8.3: Designing the Coil	148
8.4: Mono Coils	150
8.4.1: BFO Coil	150
8.4.2: Pulse Induction Coil	152
8.5: DD Coils	154
8.5.1: Windings	155
8.5.2: Shielding	156
8.5.3: Cable & Connector	156
8.5.4: Assembly & Nulling	157
8.5.5: Potting	158
8.5.6: Tweak Wire Option	158
8.5.7: Final Null & Sealing	158
8.5.8: Results	158
8.5.9: OO and 00 Coils	159
8.6: Concentric Coils	160
8.6.1: Ideal Calculations	160
8.6.2: Actual Reality	161
8.6.3: Tweaking the Null	162
8.6.4: Coil Design	162
8.6.5: Winding the Coils	163
8.6.6: Feedback Coil	163
8.6.7: Shielding — Part 1	164
8.6.8: Coil Assembly	164
8.6.9: Potting — Part 1	164
8.6.10: Shielding — Part 2	165
8.6.11: Fine Nulling	165
8.6.12: Potting — Part 2	165
8.6.13: Results	166
8.7: Coaxial Coil	166

8.8: Figure-8 Coil	167
8.9: Probe Coil	167
8.10: Water Coils	168
Explore	168
8.11: TX Resistance	168
8.12: Modified Concentric Design	169
8.13: Butterfly Coil	170
8.14: X-Null vs R-Null	171
8.15: Gold Coils	172
8.16: Multifrequency Coils	172
8.17: Automated Coil Identification	172
8.18: Alternate Shield Contacting	173
8.19: Conductors in the Coil	173
8.20: Aluminum Wire	173
Part 3: Proximity Methods	
Chapter 9: Energy Theft.	177
9.1: Overview	177
9.2: Block Diagram	178
9.3: Oscillator	178
9.4: Search Coil	180
9.5: Peak Detector	180
9.6: Threshold	181
Design: Energy-Theft Pinpointer	181
Design: VCO Pinpointer	182
Explore	185
9.7: Improving the Tempco	185
9.8: Digital Design	185
Chapter 10: The BFO	187
10.1: Overview	187
10.2: Frequency Considerations	188
10.3: Component Sensitivities	191
10.4: Coil Considerations	192
10.5: Drift & Other Annoyances	192
10.6: Tuning	193
10.7: Practical Considerations	195
Design: Classic BFO	196
10.8: Oscillator Design	196
10.9: Mixer/Filter	198
10.10: Audio	199
10.11: Power Supply	199
10.12: Search Coil	200
10.13: Calibration	200
Explore	202
10.14: Digital BFO	202
10.15: Digital Non-BFO	203
10.16: Harmonic Mixing	204
10.17: Stability	204
10.18: Discrimination	204
Chapter 11: Off-Resonance	207
11.1: Overview	207

11.2: Theory	208
11.3: Responses	210
11.4: Transmitter	211
11.5: Peak Detector	212
Design: Off-Resonance Detector	214
11.6: Calibration	214
Explore	216
11.7: TX Amplitude Control	216
11.8: Digital Design	216
Chapter 12: Phase-Locked Loop	219
12.1: Overview	220
12.2: Inside the 4046	220
12.3: Testing the 4046	221
Design: PLL Detector	222
Explore	224
12.4: Frequency Scaling	224
12.5: Reversed Roles	224
12.6: VLF BFO	225
12.7: Multifrequency Induction-Balanced VLF BFO	225
12.8: Digital PLL	226

Part 4: Induction Balance

Chapter 13: Transmit-Receive	229
13.1: Overview	229
13.2: Transmit Circuit	231
13.3: RX Circuit	231
13.4: Search Coil	233
Design: Basic TR	235
Design: Improved TR	235
Explore	238
13.5: Two-Box Detectors	238
13.6: Fisher Gemini	238
13.7: White's TM-808	239
13.8: Other Two-Box Options	239
Chapter 14: TR Discrimination	241
IB Fundamentals	242
14.1: Phase	242
14.2: Reference Signal	243
14.3: Target Signals	244
Demodulation	246
14.4: Synchronous Demodulation	246
14.5: Sampling	246
14.6: Averaging	247
14.7: Target Responses	248
14.8: Variable Discrimination	249
14.9: Polar Plots	251
14.10: Demodulator Clock	252
Remaining Circuitry	254
14.11: Retune Circuit	254
14.12: Audio	255
14.13: Power Supply	256

Design: TR-Disc	257
Explore.	261
14.14: Band-pass Filtering — Part 1	261
14.15: All-Pass Filter Tuning Range	262
14.16: Retune Revisited	262
14.17: Autotune Circuit	263
14.18: Demodulators — Part 1	264
Chapter 15: VLF Ground Balance	271
Ground Response.	272
15.1: Loss Angle	272
15.2: Frequency Response	272
15.3: Advantages of Low Frequency	272
Demodulation	273
15.4: Block Diagram	275
15.5: Demodulator Clock.	275
15.6: Hybrid VLF/TR-Disc	278
Design: VLF/TR-Discriminator.	279
Explore.	282
15.7: Parallel Detection System	282
15.8: Band-pass Filtering — Part 2	282
15.9: Demodulators — Part 2	284
15.10: Mode + Retune	285
Chapter 16: Motion VLF	287
16.1: Quadrature Demodulation.	288
16.2: Target Vectors.	291
16.3: Demod Clocks.	292
16.4: Ground + Target Responses	293
16.5: High-Pass Filter	294
16.6: Time-Domain Filter Responses	296
16.7: Ground Balance	297
16.8: Demod Clocking.	298
16.9: The G Signal	299
16.10: Salt Balance	300
16.11: Frequency Considerations.	301
Design: Motion VLF	304
16.12: Transmitter	304
16.13: Preamp	304
16.14: Demodulators	304
16.15: Motion Filters	305
16.16: Audio Circuitry.	305
16.17: Power Supplies	305
16.18: Calibration.	310
Explore.	310
16.19: Demodulators — Part 3	310
16.19.1: Gilbert Cell	310
16.19.2: Sampling Integrator	310
16.19.3: Differential Demod	311
16.19.4: White's 6000 Demod	311
16.19.5: Feedback SHA	312
16.19.6: Switched-Cap Demod	312
16.19.7: Improved Switched-Cap Demod	312

16.19.8: Tayloe Demod	312
16.20: Band-pass Filtering — Part 3	313
16.21: G Channel Demod	314
16.22: I (X) Signal Polarity	314
16.23: 4-Filter Designs	314
16.24: Demod Switch Selection	315
Chapter 17: VLF Discrimination	317
17.1: Demod Rotation	317
17.2: Ratiometric Discrimination	318
17.3: Applying Discrimination	320
Design: VLF Disc	322
17.4: Discrimination Circuitry	322
17.5: All-Metal and Mode Selection	323
17.6: Audio Circuitry	323
17.7: Complete Schematic and Calibration	328
Explore	328
17.8: Multi-Tone Audio	328
17.9: Channel Gains	329
17.10: First Derivative Designs	329
17.11: Non-Quadrature Sampling	330
Chapter 18: Digital Techniques	331
Digital Design	331
18.1: Baseband Sampling Architecture	332
18.1.1: Choosing the ADC	333
18.1.2: Sample Rate	334
18.1.3: Oversampling and Dithering	334
18.2: The Micro	335
18.2.1: Processing Loop Rate	335
18.2.2: Processing Loop Control	336
18.3: Timer Requirements	337
Digital Processing	338
18.4: Input Filter	338
18.5: Signal Arrays	339
18.6: G Channel	339
18.7: Derivatives	339
18.8: Target Calculations	340
18.9: Ground Tracking	342
18.10: Discrimination	343
18.11: Misc. Processing	344
18.11.1: Overload Detection	344
18.11.2: Pinpointing	344
18.11.3: Coil Identification	344
18.11.4: Coil Accelerometer	344
User Interface	344
18.12: Inputs	345
18.12.1: Keypad	345
18.12.2: Knobs	346
18.12.3: Touchscreen	346
18.13: Audio	346
18.13.1: Pinpoint Audio	348
18.13.2: Tone ID	348

18.13.3: Mixed Mode Audio	349
18.13.4: Depth Modulation	350
18.13.5: Headphones	350
18.13.6: Wireless	350
18.13.7: Tactile Feedback	351
18.14: Display	351
18.14.1: Segmented and Graphics LCDs	351
18.14.2: TID and VDI	352
18.14.3: Spectral Meter	354
18.14.4: Category Meter	355
18.14.5: Discrimination	356
18.14.6: Sweep Averaging	356
18.14.7: Confidence Meter	356
18.14.8: Depth Readout	356
18.14.9: Ground Meter	357
18.14.10: Modes and Menus	358
18.14.11: Other Display Elements	358
18.15: Saving Settings	359
Explore.	359
18.16: Direct Sampling	359
18.17: Digital Demodulation	359
18.18: Hodograph.	360
18.19: Static Mode Improvements.	360
18.20: Special Coil Considerations	361
18.21: The Ultimate Programmable Detector	361
Part 5: Pulse Induction	
Chapter 19: Pulse Induction.	365
19.1: Overview.	365
Transmitter.	365
19.2: Flyback	368
19.3: An Example	369
19.4: Target Responses	371
19.5: Practical Transmit Switches	371
Receiver.	372
19.6: Preamp	373
19.7: Sampling	374
19.8: Self-Adjusting Threshold (SAT).	376
19.9: Gain & Threshold	377
19.10: Audio.	377
Complete (Conceptual) Circuit	377
Explore.	378
19.11: Anti-Interference Coils	378
Chapter 20: Basic PI Design.	381
Transmitter.	381
20.1: The Coil	381
20.2: Transmit Driver.	382
20.3: Damping	383
Receiver.	383
20.4: Preamp	383
20.5: Power Supply	384

20.6: Sampling & Gain	386
20.7: Audio	387
Clocking	389
Design: Basic PI (Pulse-1)	390
Explore	394
20.8: Coil	394
20.9: Adjustable Damping	394
20.10: Coil Switch	394
20.11: Preamp	395
20.12: Demod	395
20.13: VSAT	396
20.14: Clock	397
Chapter 21: Improved PI Design	399
Modernized Platform	399
21.1: Transmitter	399
21.2: Power Supply	400
21.3: Receiver Back-End	402
21.4: Micro	403
Design: Improved PI (Pulse-2)	406
Earth Field Effect	406
21.5: High-Pass Filtering	407
21.6: Correlated Double Sampling	407
Design: Improved PI (Pulse-3)	409
Optimizing	412
21.7: Decay Speed	412
21.8: Other TX Considerations	412
21.9: TX Pulse Rate & Width	413
21.10: Sample Pulse	413
21.11: Supply Voltage	414
Explore	415
21.12: Flat-topping	415
21.13: Avalanching	416
21.14: Capacitance Reduction	417
21.15: Snubbing	418
21.16: Improved TX Switch Drive	419
21.17: Alternate TX Switch Drive	420
21.18: MOSFET Drive voltage	420
21.19: Clamp Performance	420
21.20: Two-Stage Preamp	421
Chapter 22: Ground Balanced PI	423
22.1: Viscous Remanence Magnetization	423
22.2: Implementation	425
22.3: Signal Responses	426
22.4: Back-End & Audio	427
Design: Ground Balanced PI (Pulse-4)	429
Explore	433
22.5: PWM SAT Control	433
22.6: Target Hole Selection	433
22.7: 4-Channel “no hole” PI	433
22.8: PWM Ground Balance	435
22.9: Digital Design	436

22.10: Direct Sampling	436
22.11: Split Coil	437
Chapter 23: Bipolar PI	439
Transmitter	440
23.1: H-Bridge Design	441
23.2: Differential Coil Design	445
Receiver	446
23.3: Demods & GB	447
23.4: Audio Stage	447
Design: Bipolar PI (Pulse-5)	454
Explore	455
23.5: Differential Dual Coil Variants	455
23.6: Simultaneous Differential Pulsing	455
23.7: TDI Audio	455
23.8: Security Walk-Through	456
Part 6: Advanced Methods	
Chapter 24: Multifrequency	461
24.1: Overview	461
24.2: Case Studies	463
24.2.1: Fisher CZ	463
24.2.2: White's DFX	464
24.2.3: Minelab BBS/FBS	465
24.2.4: White's V3	466
24.2.5: Minelab Equinox	467
24.2.6: Boosted Sequential Multifrequency	468
24.3: Multifrequency Signals	469
24.3.1: Measuring MF Target Responses	469
24.3.2: Ground Response	470
24.3.3: Salt	470
24.3.4: Iron Responses	470
24.3.5: Eddy Responses	472
24.4: Multifrequency Processing	472
24.4.1: Correlated Processing	472
24.4.2: Salt Notching	473
24.4.3: Composite Processing	474
24.5: Multifrequency Efficiency	476
24.6: Multifrequency Design	477
24.6.1: Transmitter	477
24.6.2: Preamp	477
24.6.3: Channel Filters	478
24.6.4: Demods	478
24.6.5: Remainder	478
Explore	479
24.7: Dual Preamps	479
24.8: Narrowband Demodulators	479
24.9: Asynchronous Demodulation	479
24.10: Moreland-Kelley Filter	480
Chapter 25: Advanced PI	483
Multi-Period PI	483
25.1: Proportional Timing	484

25.2: Multi-Voltage Drive	484
25.3: Equalized Multi-Voltage Drive	485
25.4: Multi-Step Drive	487
25.5: Two-Slope Ground Balance	489
25.6: Noise	490
Constant-Current PI	490
25.7: Brute-Force Drive	491
25.8: Recycling Kickstart Methods	492
25.9: Square Wave Drive	493
25.10: Current Control	495
25.11: Switching Losses	495
Explore	496
25.12: Flyback Isolation	496
25.13: Dynamic Damping	498
25.14: Iron Discrimination	498
Chapter 26: Hybrid Methods	501
Half-Sine	501
26.1: Transmitter	501
26.2: Hybrid Response	502
26.3: Efficiency	503
26.4: Slew Rate	503
26.5: Ideal Target Responses	504
26.6: Actual Target Responses	505
26.7: Receiver	506
26.8: Conceptual Circuit	507
26.9: Processing	508
Truncated Half-Sine	508
26.10: Transmitter	509
26.11: Receiver	510
Other Hybrids	510
26.12: PI-TX Response	510
26.13: Gold Sweeper	511
26.14: Pulse Devil	512
26.15: Voodoo	512
Explore	513
26.16: Multifrequency Half-Sine	513
26.17: Faking a Hybrid	514

Part 7: Leftovers

Chapter 27: Oddball Circuits	519
27.1: Thomas Scarborough	519
27.1.1: Beat Balance	519
27.1.2: CCO Metal Detector	520
27.2: Balanced Inductor Design	520
27.3: Minelab Go Find	521
27.4: Buckless Concentric Coil	521
27.5: White's Mono-Coil TR	522
27.6: Tarsacci	522
27.7: Inductive Sensor Chips	523
27.7.1: CS209A	523
27.7.2: LDC1000	523

Chapter 28: Things & Stuff & Junk	525
28.1: Is it an antenna?	525
28.2: Transmit Power	525
28.3: FCC Regulations	526
28.4: Power Limits	528
28.5: Metal in the Coil	528
28.6: Power Line Interference	529
28.7: Detector Cross-Talk Interference	530
28.8: Silent EMI	530
28.9: The Halo Effect, Part 1	531
28.10: The Halo Effect, Part 2	531
28.11: Treasure Hunting Methods	532
28.12: Treasure Hunting Mythology	532
28.13: Great Ideas	533
28.14: Going Solo	534
28.15: Counterfeiting	535

Part 8: Appendices

Appendix A: Magnetic Field Probe	539
A.1: Theory	539
A.2: Sensor	540
A.3: Remaining Design	541
A.4: Construction	544
A.5: Calibration	546
A.6: Usage	546
Appendix B: Coil Calculations	549
B.1: Solenoidal Coils	549
B.2: Short Coils	550
B.3: General Short/Long Coils	551
B.4: Spiral Inductors	551
B.5: Accuracy	551
B.6: Coil Calculator	552
B.7: Non-Circular Coils	552
Appendix C: PI Math	553
The Transmit Side	553
C.1: TX Turn-On Response	553
C.2: TX Turn-Off Response	555
The Target Side	560
C.3: TX Turn-On Eddies	560
C.4: TX Turn-Off Eddies	562
C.5: Complete Eddy Response	564
C.6: Target Response vs Turn-Off Slew Rate	565
The Receive Side	567
C.7: RX Coil Response	567
C.8: EFE Sample	568
C.9: Ground Balance	570
C.10: Power Consumption	572
Appendix D: Resources	573
Web Sites	573
Books	574
Research Papers	574

Periodical Articles	576
Other	582
Appendix E: Patents	583
E.1: The Patent Minefield	583
E.2: Patent Requirements	584
Patents	585
E.3: Proximity Methods	585
E.4: Induction Balance (TR/VLF) Methods	586
E.5: Multifrequency	589
E.6: Pulse Induction/Time Domain	589
E.7: Hybrid/Other Methods	591
E.8: Coils	591
E.9: Eddy techniques	593
E.10: DSP Methods	593
E.11: Security	593
E.12: Mine Detection	594
E.13: Misc.	594
E.14: Pre-1970	596
Appendix F: Glossary	597
Index	601