

---

# Table of Contents

---

## Part 1: Fundamentals

|  |    |
|--|----|
| <b>Chapter 1: History</b> .....            | 9  |
| The People .....                           | 9  |
| 1.1: Hans Christian Ørsted .....           | 9  |
| 1.2: Michael Faraday .....                 | 9  |
| 1.3: Heinrich Wilhelm Dove .....           | 9  |
| 1.4: David Hughes .....                    | 9  |
| 1.5: Alexander Graham Bell .....           | 10 |
| 1.6: Other Early Inventors .....           | 11 |
| 1.7: Gerhard Fisher .....                  | 13 |
| 1.8: Later Contributors .....              | 13 |
| The Applications .....                     | 14 |
| 1.9: Military Use .....                    | 14 |
| 1.10: Commercial & Industrial Use .....    | 15 |
| 1.11: Treasure Hunting .....               | 15 |
| The Technologies .....                     | 16 |
| 1.12: BFO .....                            | 16 |
| 1.13: IB .....                             | 17 |
| 1.14: PI .....                             | 17 |
| The Companies .....                        | 17 |
| 1.15: Fisher .....                         | 18 |
| 1.16: White's .....                        | 18 |
| 1.17: Garrett .....                        | 19 |
| 1.18: Bounty Hunter .....                  | 20 |
| 1.19: Compass .....                        | 21 |
| 1.20: Teknetics .....                      | 21 |
| 1.21: C&G/Tesoro .....                     | 22 |
| 1.22: Minelab .....                        | 22 |
| 1.23: XP .....                             | 23 |
| 1.24: Nokta .....                          | 23 |
| 1.25: Others .....                         | 23 |
| <b>Chapter 2: Types of Detectors</b> ..... | 25 |
| Proximity Effect .....                     | 25 |
| 2.1: BFO .....                             | 25 |
| 2.2: Energy Theft .....                    | 26 |
| 2.3: Off-Resonance .....                   | 26 |
| 2.4: PLL .....                             | 26 |
| Induction Balance .....                    | 27 |
| 2.5: IB .....                              | 27 |
| 2.6: TR .....                              | 27 |
| 2.7: RF .....                              | 28 |

|   |           |
|---|-----------|
| 2.8: VLF  | 28        |
| 2.9: VLF/TR   | 29        |
| 2.10: Multifrequency                                      | 29        |
| Pulse Induction   | 30        |
| 2.11: Basic PI  | 30        |
| 2.12: Ground Balance PI                                   | 30        |
| 2.13: Other PI Developments                               | 30        |
| Other Jargon  | 31        |
| 2.14: Continuous-Time vs Discrete-Time: Transmitters      | 31        |
| 2.15: Continuous-Time vs Discrete-Time: Demodulators      | 32        |
| 2.16: Continuous-Time vs Discrete-Time: Signal Processing | 33        |
| 2.17: Frequency Domain vs Time Domain                     | 33        |
| 2.18: Synchronous Demodulation                            | 34        |
| 2.19: Direct Sampling                                     | 35        |
| 2.20: Hybrid Designs                                      | 35        |
| 2.21: The Future  | 36        |
| <b>Chapter 3: Magnetics &amp; Induction</b>               | <b>37</b> |
| Magnetics   | 37        |
| 3.1: Static Magnetic Fields                               | 37        |
| 3.2: Alternating Magnetic Fields                          | 39        |
| 3.3: Coil Fields  | 40        |
| Induction   | 43        |
| 3.4: Induction Balance                                    | 44        |
| Explore   | 47        |
| 3.5: Compass Experiments                                  | 47        |
| 3.6: Visualizing Magnetic Fields                          | 47        |
| <b>Chapter 4: Target Responses</b>                        | <b>49</b> |
| Magnetic Responses  | 49        |
| 4.1: Magnetic Lag   | 49        |
| 4.2: Ground vs Iron                                       | 52        |
| 4.3: Hot Rocks  | 53        |
| 4.4: Viscous Magnetic Response                            | 53        |
| 4.5: Earth Field  | 54        |
| Eddy Responses  | 54        |
| 4.6: The Physics of Eddy Currents                         | 57        |
| 4.7: Eddy Depth Distribution                              | 58        |
| 4.8: Skin Effect  | 59        |
| 4.9: Eddy Surface Distribution                            | 60        |
| 4.10: Target Field Phase                                  | 62        |
| 4.11: Target Field Amplitude                              | 64        |
| 4.12: RL Target Model                                     | 64        |
| 4.13: Wire Loop Tau                                       | 65        |
| 4.14: Salt Water  | 67        |
| Transmitter Effects                                       | 67        |
| Explore   | 69        |
| 4.15: Alloy Conductivities                                | 69        |
| 4.16: Practical Test Targets                              | 69        |
| 4.17: Measuring Target Taus                               | 71        |
| 4.18: Fun With Eddy Currents                              | 73        |
| <b>Chapter 5: Complex Responses</b>                       | <b>75</b> |
| Problem Targets   | 75        |
| 5.1: Composite Responses — Iron                           | 75        |
| 5.2: Positional Quirks                                    | 77        |
| 5.3: Composite Responses — Co-Located Targets             | 79        |

|  |    |
|--|----|
| 5.4: Adjacent Targets . . . . .                              | 80 |
| 5.5: Difficult Metals . . . . .                              | 81 |
| 5.6: Composite Responses — Multiple Domain Targets . . . . . | 81 |
| 5.7: Size & Shape Effects . . . . .                          | 82 |
| Time Domain Responses . . . . .                              | 83 |
| 5.8: Ramp Response . . . . .                                 | 83 |
| 5.9: Step Response . . . . .                                 | 86 |
| 5.10: Exponential Response . . . . .                         | 88 |
| Explore . . . . .  | 89 |
| 5.11: Testing Recovery Speed . . . . .                       | 89 |
| 5.12: The Monte Nail Board . . . . .                         | 89 |
| 5.13: Simple Test Jig . . . . .                              | 89 |
| 5.14: Gold versus Aluminum . . . . .                         | 91 |

## Part 2: Coils

|  |     |
|--|-----|
| <b>Chapter 6: Coil Types</b> . . . . .       | 95  |
| Planar Coils . . . . .                       | 95  |
| 6.1: Mono Coil . . . . .                     | 95  |
| 6.2: Double-O Coil . . . . .                 | 95  |
| 6.3: Double-D Coil . . . . .                 | 96  |
| 6.4: Other Overlaps . . . . .                | 97  |
| 6.5: Concentric Coil . . . . .               | 98  |
| 6.6: Omega Coil . . . . .                    | 99  |
| 6.7: Figure-8 Coil . . . . .                 | 100 |
| 6.8: Butterfly Coil . . . . .                | 101 |
| Non-Planar Coils . . . . .                   | 101 |
| 6.9: Coaxial Coil . . . . .                  | 101 |
| 6.10: Orthogonal Coil . . . . .              | 103 |
| Dual Coils . . . . .                         | 105 |
| Explore . . . . .                            | 106 |
| 6.11: Coil Sizes & Weights . . . . .         | 106 |
| <b>Chapter 7: Coil Performance</b> . . . . . | 109 |
| Transmit . . . . .                           | 109 |
| 7.1: Using the Probe . . . . .               | 109 |
| 7.2: Comparative Measurements . . . . .      | 110 |
| Receive . . . . .                            | 112 |
| 7.3: Receive Coil Physics . . . . .          | 112 |
| 7.4: Detection Patterns . . . . .            | 113 |
| 7.5: Concentric Coils . . . . .              | 115 |
| 7.6: Overlapped Coils . . . . .              | 117 |
| 7.7: Coaxial Coils . . . . .                 | 119 |
| 7.8: Figure-8 Coils . . . . .                | 119 |
| Other Considerations . . . . .               | 120 |
| 7.9: Mineralization & Lift-Off . . . . .     | 120 |
| 7.10: Target Separation . . . . .            | 122 |
| 7.11: EMI . . . . .                          | 122 |
| 7.12: Spacial Alignment . . . . .            | 123 |
| Explore . . . . .                            | 124 |
| 7.13: More Power . . . . .                   | 124 |
| 7.14: The Math of Depth: Part 1 . . . . .    | 124 |
| 7.15: The Math of Depth: Part 2 . . . . .    | 124 |
| 7.16: RX Coil Size Revisited . . . . .       | 125 |
| <b>Chapter 8: Building Coils</b> . . . . .   | 127 |
| 8.1: Coil Windings . . . . .                 | 127 |

|                                     |     |
|-------------------------------------|-----|
| 8.1.1: Coil Parametrics             | 127 |
| 8.1.2: Wire                         | 129 |
| 8.1.3: Coil Windings                | 130 |
| 8.1.4: Winding Coils                | 133 |
| 8.1.5: Bondable Wire                | 133 |
| 8.1.6: Automated Winder             | 134 |
| 8.2: Other Elements                 | 134 |
| 8.2.1: Coil Shell                   | 135 |
| 8.2.2: Potato Chipping              | 135 |
| 8.2.3: Cable                        | 136 |
| 8.2.4: Connector                    | 137 |
| 8.2.5: Shielding                    | 137 |
| 8.2.6: Stabilization                | 140 |
| 8.3: Designing the Coil             | 141 |
| 8.4: Mono Coils                     | 143 |
| 8.4.1: BFO Coil                     | 143 |
| 8.4.2: Pulse Induction Coil         | 145 |
| 8.5: DD Coils                       | 147 |
| 8.5.1: Windings                     | 148 |
| 8.5.2: Shielding                    | 149 |
| 8.5.3: Cable & Connector            | 149 |
| 8.5.4: Assembly & Nulling           | 150 |
| 8.5.5: Potting                      | 151 |
| 8.5.6: Tweak Wire Option            | 151 |
| 8.5.7: Final Null & Sealing         | 151 |
| 8.5.8: Results                      | 151 |
| 8.5.9: OO and 00 Coils              | 152 |
| 8.6: Concentric Coils               | 153 |
| 8.6.1: Ideal Calculations           | 153 |
| 8.6.2: Actual Reality               | 154 |
| 8.6.3: Tweaking the Null            | 154 |
| 8.6.4: Coil Design                  | 155 |
| 8.6.5: Winding the Coils            | 156 |
| 8.6.6: Feedback Coil                | 156 |
| 8.6.7: Shielding — Part 1           | 156 |
| 8.6.8: Coil Assembly                | 157 |
| 8.6.9: Potting — Part 1             | 157 |
| 8.6.10: Shielding — Part 2          | 157 |
| 8.6.11: Fine Nulling                | 157 |
| 8.6.12: Potting — Part 2            | 158 |
| 8.6.13: Results                     | 158 |
| 8.7: Coaxial Coil                   | 159 |
| 8.8: Figure-8 Coil                  | 159 |
| 8.9: Probe Coil                     | 159 |
| 8.10: Water Coils                   | 160 |
| Explore                             | 161 |
| 8.11: TX Resistance                 | 161 |
| 8.12: Modified Concentric Design    | 162 |
| 8.13: Butterfly Coil                | 163 |
| 8.14: X-Null vs R-Null              | 163 |
| 8.15: Gold Coils                    | 164 |
| 8.16: Multifrequency Coils          | 164 |
| 8.17: Automated Coil Identification | 165 |
| 8.18: Alternate Shield Contacting   | 165 |

|  |     |
|--|-----|
| 8.19: Conductors in the Coil . . . . . | 165 |
| 8.20: Aluminum Wire . . . . .          | 166 |

## Part 3: Proximity Methods

|  |     |
|--|-----|
| <b>Chapter 9: Energy Theft</b> . . . . .       | 169 |
| 9.1: Overview . . . . .                        | 169 |
| 9.2: Block Diagram . . . . .                   | 170 |
| 9.3: Oscillator . . . . .                      | 170 |
| 9.4: Search Coil . . . . .                     | 171 |
| 9.5: Peak Detector . . . . .                   | 172 |
| 9.6: Threshold . . . . .                       | 173 |
| Design: Energy-Theft Pinpointer . . . . .      | 173 |
| Design: VCO Pinpointer . . . . .               | 174 |
| Explore . . . . .                              | 177 |
| 9.7: Improving the Tempco . . . . .            | 177 |
| 9.8: Digital Design . . . . .                  | 177 |
| <b>Chapter 10: The BFO</b> . . . . .           | 179 |
| 10.1: Overview . . . . .                       | 179 |
| 10.2: Frequency Considerations . . . . .       | 180 |
| 10.3: Component Sensitivities . . . . .        | 183 |
| 10.4: Coil Considerations . . . . .            | 183 |
| 10.5: Drift & Other Annoyances . . . . .       | 184 |
| 10.6: Tuning . . . . .                         | 185 |
| 10.7: Practical Considerations . . . . .       | 187 |
| Design: Classic BFO . . . . .                  | 187 |
| 10.8: Oscillator Design . . . . .              | 187 |
| 10.9: Mixer/Filter . . . . .                   | 189 |
| 10.10: Audio . . . . .                         | 190 |
| 10.11: Power Supply . . . . .                  | 190 |
| 10.12: Search Coil . . . . .                   | 191 |
| 10.13: Calibration . . . . .                   | 191 |
| Explore . . . . .                              | 193 |
| 10.14: Digital BFO . . . . .                   | 193 |
| 10.15: Digital Non-BFO . . . . .               | 194 |
| 10.16: Discrimination . . . . .                | 195 |
| 10.17: Harmonic Mixing . . . . .               | 196 |
| 10.18: Stability . . . . .                     | 196 |
| <b>Chapter 11: Off-Resonance</b> . . . . .     | 197 |
| 11.1: Overview . . . . .                       | 197 |
| 11.2: Theory . . . . .                         | 198 |
| 11.3: Responses . . . . .                      | 200 |
| 11.4: Transmitter . . . . .                    | 201 |
| 11.5: Peak Detector . . . . .                  | 202 |
| Design: Off-Resonance Detector . . . . .       | 204 |
| 11.6: Calibration . . . . .                    | 204 |
| Explore . . . . .                              | 204 |
| 11.7: TX Amplitude Control . . . . .           | 204 |
| 11.8: Digital Design . . . . .                 | 206 |
| <b>Chapter 12: Phase-Locked Loop</b> . . . . . | 207 |
| 12.1: Overview . . . . .                       | 208 |
| 12.2: Inside the 4046 . . . . .                | 208 |
| 12.3: Testing the 4046 . . . . .               | 208 |
| Design: PLL Detector . . . . .                 | 209 |
| Explore . . . . .                              | 212 |

|   |     |
|---|-----|
| 12.4: Frequency Scaling . . . . .                         | 212 |
| 12.5: Reversed Roles . . . . .                            | 212 |
| 12.6: VLF BFO . . . . .                                   | 213 |
| 12.7: Multifrequency Induction-Balanced VLF BFO . . . . . | 213 |
| 12.8: Digital PLL . . . . .                               | 214 |

## Part 4: Induction Balance

|   |     |
|---|-----|
| <b>Chapter 13: Transmit-Receive</b> . . . . .   | 217 |
| 13.1: Overview . . . . .                        | 217 |
| 13.2: Transmit Circuit . . . . .                | 219 |
| 13.3: RX Circuit . . . . .                      | 219 |
| 13.4: Search Coil . . . . .                     | 221 |
| Design: Basic TR . . . . .                      | 221 |
| Design: Improved TR . . . . .                   | 223 |
| Explore . . . . .                               | 224 |
| 13.5: Two-Box Detectors . . . . .               | 224 |
| 13.6: White's TM-808 . . . . .                  | 226 |
| 13.7: Fisher Gemini . . . . .                   | 226 |
| 13.8: Other Two-Box Options . . . . .           | 227 |
| <b>Chapter 14: TR Discrimination</b> . . . . .  | 229 |
| IB Fundamentals . . . . .                       | 230 |
| 14.1: Phase . . . . .                           | 230 |
| 14.2: Reference Signal . . . . .                | 231 |
| 14.3: Target Signals . . . . .                  | 232 |
| Demodulation . . . . .                          | 233 |
| 14.4: Synchronous Demodulation . . . . .        | 234 |
| 14.5: Sampling . . . . .                        | 234 |
| 14.6: Averaging . . . . .                       | 235 |
| 14.7: Target Responses . . . . .                | 235 |
| 14.8: Variable Discrimination . . . . .         | 236 |
| 14.9: Polar Plots . . . . .                     | 239 |
| 14.10: Demodulator Clock . . . . .              | 239 |
| Remaining Circuitry . . . . .                   | 241 |
| 14.11: Retune Circuit . . . . .                 | 242 |
| 14.12: Audio . . . . .                          | 242 |
| 14.13: Power Supply . . . . .                   | 243 |
| Design: TR-Disc . . . . .                       | 244 |
| Explore . . . . .                               | 248 |
| 14.14: Band-pass Filtering — Part 1 . . . . .   | 248 |
| 14.15: All-Pass Filter Tuning Range . . . . .   | 248 |
| 14.16: Retune Revisited . . . . .               | 249 |
| 14.17: Autotune Circuit . . . . .               | 250 |
| 14.18: Demodulators — Part 1 . . . . .          | 250 |
| <b>Chapter 15: VLF Ground Balance</b> . . . . . | 257 |
| Ground Response . . . . .                       | 258 |
| 15.1: Loss Angle . . . . .                      | 258 |
| 15.2: Frequency Response . . . . .              | 258 |
| 15.3: Advantages of Low Frequency . . . . .     | 258 |
| Demodulation . . . . .                          | 259 |
| 15.4: Block Diagram . . . . .                   | 261 |
| 15.5: Demodulator Clock . . . . .               | 261 |
| 15.6: Hybrid VLF/TR-Disc . . . . .              | 264 |
| Design: VLF/TR-Discriminator . . . . .          | 265 |
| Explore . . . . .                               | 268 |

|  |            |
|--|------------|
| 15.7: Parallel Detection System . . . . .          | 268        |
| 15.8: Band-pass Filtering — Part 2 . . . . .       | 268        |
| 15.9: Demodulators — Part 2 . . . . .              | 269        |
| 15.10: Mode + Retune . . . . .                     | 271        |
| <b>Chapter 16: Motion VLF . . . . .</b>            | <b>273</b> |
| 16.1: Quadrature Demodulation . . . . .            | 274        |
| 16.2: Target Vectors . . . . .                     | 277        |
| 16.3: Demod Clocks . . . . .                       | 278        |
| 16.4: Ground + Target Responses . . . . .          | 279        |
| 16.5: High-Pass Filter . . . . .                   | 280        |
| 16.6: Time-Domain Filter Responses . . . . .       | 282        |
| 16.7: Ground Balance . . . . .                     | 283        |
| 16.8: Demod Clocking . . . . .                     | 283        |
| 16.9: The G Signal . . . . .                       | 285        |
| 16.10: Salt Balance . . . . .                      | 286        |
| 16.11: Frequency Considerations . . . . .          | 287        |
| Design: Motion VLF . . . . .                       | 289        |
| 16.12: Transmitter . . . . .                       | 289        |
| 16.13: Preamp . . . . .                            | 289        |
| 16.14: Demodulators . . . . .                      | 289        |
| 16.15: Motion Filters . . . . .                    | 290        |
| 16.16: Audio Circuitry . . . . .                   | 290        |
| 16.17: Power Supplies . . . . .                    | 290        |
| 16.18: Calibration . . . . .                       | 295        |
| Explore . . . . .                                  | 295        |
| 16.19: Demodulators — Part 3 . . . . .             | 295        |
| 16.19.1: Gilbert Cell . . . . .                    | 295        |
| 16.19.2: Sampling Integrator . . . . .             | 295        |
| 16.19.3: Differential SHA . . . . .                | 296        |
| 16.19.4: White's 6000 Demod . . . . .              | 296        |
| 16.19.5: Feedback SHA . . . . .                    | 296        |
| 16.19.6: Switched-Cap Demod . . . . .              | 297        |
| 16.19.7: Improved Switched-Cap Demod . . . . .     | 297        |
| 16.19.8: Tayloe Demod . . . . .                    | 297        |
| 16.20: Band-pass Filtering — Part 3 . . . . .      | 298        |
| 16.21: G Channel Demod . . . . .                   | 299        |
| 16.22: 4-Filter Designs . . . . .                  | 299        |
| 16.23: I (X) Signal Polarity . . . . .             | 300        |
| 16.24: Demod Switch Selection . . . . .            | 300        |
| <b>Chapter 17: VLF Discrimination . . . . .</b>    | <b>301</b> |
| 17.1: Demod Rotation . . . . .                     | 301        |
| 17.2: Ratiometric Discrimination . . . . .         | 302        |
| 17.3: Applying Discrimination . . . . .            | 304        |
| Design: VLF Disc. . . . .                          | 305        |
| 17.4: Discrimination Circuitry . . . . .           | 306        |
| 17.5: All-Metal and Mode Selection . . . . .       | 306        |
| 17.6: Audio Circuitry . . . . .                    | 307        |
| 17.7: Complete Schematic and Calibration . . . . . | 307        |
| Explore . . . . .                                  | 312        |
| 17.8: Multi-Tone Audio . . . . .                   | 312        |
| 17.9: Channel Gains . . . . .                      | 312        |
| 17.10: First Derivative Designs . . . . .          | 313        |
| 17.11: Non-Quadrature Sampling . . . . .           | 313        |

|   |     |
|---|-----|
| <b>Chapter 18: Digital Techniques</b> ..... | 315 |
| Digital Design .....                        | 315 |
| 18.1: Baseband Sampling Architecture .....  | 316 |
| 18.1.1: Choosing the ADC .....              | 317 |
| 18.1.2: Sample Rate .....                   | 318 |
| 18.1.3: Oversampling and Dithering .....    | 318 |
| 18.2: The Micro .....                       | 319 |
| 18.2.1: Processing Loop Rate .....          | 319 |
| 18.2.2: Processing Loop Control .....       | 320 |
| 18.3: Timer Requirements .....              | 321 |
| Digital Processing .....                    | 322 |
| 18.4: Input Filter .....                    | 322 |
| 18.5: Signal Arrays .....                   | 322 |
| 18.6: G Channel .....                       | 323 |
| 18.7: Derivatives .....                     | 323 |
| 18.8: Target Calculations .....             | 324 |
| 18.9: Ground Tracking .....                 | 325 |
| 18.10: Discrimination .....                 | 327 |
| 18.11: Misc. Processing .....               | 327 |
| 18.11.1: Overload Detection .....           | 327 |
| 18.11.2: Pinpointing .....                  | 327 |
| 18.11.3: Coil Identification .....          | 328 |
| 18.11.4: Coil Accelerometer .....           | 328 |
| User Interface .....                        | 328 |
| 18.12: Inputs .....                         | 328 |
| 18.12.1: Keypad .....                       | 328 |
| 18.12.2: Knobs .....                        | 329 |
| 18.12.3: Touchscreen .....                  | 330 |
| 18.13: Audio .....                          | 330 |
| 18.13.1: Pinpoint Audio .....               | 331 |
| 18.13.2: Tone ID .....                      | 331 |
| 18.13.3: Mixed Mode Audio .....             | 333 |
| 18.13.4: Depth Modulation .....             | 333 |
| 18.13.5: Headphones .....                   | 333 |
| 18.13.6: Wireless .....                     | 333 |
| 18.13.7: Tactile Feedback .....             | 334 |
| 18.14: Display .....                        | 334 |
| 18.14.1: Segmented and Graphics LCDs .....  | 334 |
| 18.14.2: TID and VDI .....                  | 335 |
| 18.14.3: Spectral Meter .....               | 337 |
| 18.14.4: Category Meter .....               | 338 |
| 18.14.5: Discrimination .....               | 338 |
| 18.14.6: Sweep Averaging .....              | 339 |
| 18.14.7: Confidence Meter .....             | 339 |
| 18.14.8: Depth Readout .....                | 339 |
| 18.14.9: Ground Meter .....                 | 340 |
| 18.14.10: Modes and Menus .....             | 340 |
| 18.14.11: Other Display Elements .....      | 341 |
| 18.15: Saving Settings .....                | 341 |
| Explore .....                               | 342 |
| 18.16: Direct Sampling .....                | 342 |
| 18.17: Digital Demodulation .....           | 342 |
| 18.18: Hodograph .....                      | 343 |
| 18.19: Static Mode Improvements .....       | 343 |



|   |     |
|---|-----|
| 18.20: Special Coil Considerations . . . . .        | 343 |
| 18.21: The Ultimate Programmable Detector . . . . . | 344 |

## Part 5: Pulse Induction

|   |     |
|---|-----|
| <b>Chapter 19: Pulse Induction</b> . . . . .    | 347 |
| 19.1: Overview . . . . .                        | 347 |
| Transmitter . . . . .                           | 347 |
| 19.2: Flyback . . . . .                         | 350 |
| 19.3: An Example . . . . .                      | 351 |
| 19.4: Target Responses . . . . .                | 353 |
| 19.5: Practical Transmit Switches . . . . .     | 353 |
| Receiver . . . . .                              | 354 |
| 19.6: Preamp . . . . .                          | 354 |
| 19.7: Sampling . . . . .                        | 355 |
| 19.8: Self-Adjusting Threshold (SAT) . . . . .  | 357 |
| 19.9: Gain & Threshold . . . . .                | 358 |
| 19.10: Audio . . . . .                          | 358 |
| Complete (Conceptual) Circuit . . . . .         | 359 |
| Explore . . . . .                               | 360 |
| 19.11: Anti-Interference Coils . . . . .        | 360 |
| <b>Chapter 20: Basic PI Design</b> . . . . .    | 363 |
| Transmitter . . . . .                           | 363 |
| 20.1: The Coil . . . . .                        | 363 |
| 20.2: Transmit Driver . . . . .                 | 364 |
| 20.3: Damping . . . . .                         | 365 |
| Receiver . . . . .                              | 365 |
| 20.4: Preamp . . . . .                          | 365 |
| 20.5: Power Supply . . . . .                    | 366 |
| 20.6: Sampling & Gain . . . . .                 | 368 |
| 20.7: Audio . . . . .                           | 368 |
| Clocking . . . . .                              | 370 |
| Design: Basic PI (Pulse-1) . . . . .            | 374 |
| Explore . . . . .                               | 375 |
| 20.8: Coil . . . . .                            | 375 |
| 20.9: Adjustable Damping . . . . .              | 375 |
| 20.10: Coil Switch . . . . .                    | 375 |
| 20.11: Preamp . . . . .                         | 375 |
| 20.12: Demod . . . . .                          | 376 |
| 20.13: VSAT . . . . .                           | 377 |
| 20.14: Clock . . . . .                          | 377 |
| <b>Chapter 21: Improved PI Design</b> . . . . . | 379 |
| Modernized Platform . . . . .                   | 379 |
| 21.1: Transmitter . . . . .                     | 379 |
| 21.2: Power Supply . . . . .                    | 380 |
| 21.3: Receiver Back-End . . . . .               | 381 |
| 21.4: Micro . . . . .                           | 382 |
| Design: Improved PI (Pulse-2) . . . . .         | 383 |
| Earth Field Effect . . . . .                    | 386 |
| 21.5: High-Pass Filtering . . . . .             | 387 |
| 21.6: Correlated Double Sampling . . . . .      | 387 |
| Design: Improved PI (Pulse-3) . . . . .         | 389 |
| Optimizing . . . . .                            | 392 |
| 21.7: Decay Speed . . . . .                     | 392 |
| 21.8: Other TX Considerations . . . . .         | 392 |

|  |            |
|--|------------|
| 21.9: TX Pulse Rate & Width . . . . .            | 393        |
| 21.10: Sample Pulse . . . . .                    | 393        |
| 21.11: Supply Voltage . . . . .                  | 394        |
| Explore . . . . .                                | 395        |
| 21.12: Flat-topping . . . . .                    | 395        |
| 21.13: Avalanching. . . . .                      | 396        |
| 21.14: Capacitance Reduction . . . . .           | 396        |
| 21.15: Snubbing . . . . .                        | 398        |
| 21.16: Improved TX Switch Drive . . . . .        | 399        |
| 21.17: Alternate TX Switch Drive . . . . .       | 399        |
| 21.18: MOSFET Drive voltage. . . . .             | 400        |
| 21.19: Clamp Performance . . . . .               | 400        |
| 21.20: Dual Preamp . . . . .                     | 401        |
| <b>Chapter 22: Ground Balanced PI. . . . .</b>   | <b>403</b> |
| 22.1: Viscous Remanence Magnetization. . . . .   | 403        |
| 22.2: Implementation . . . . .                   | 405        |
| 22.3: Signal Responses . . . . .                 | 406        |
| 22.4: Back-End & Audio . . . . .                 | 407        |
| Design: Ground Balanced PI (Pulse-4) . . . . .   | 409        |
| Explore . . . . .                                | 413        |
| 22.5: PWM SAT Control . . . . .                  | 413        |
| 22.6: Target Hole Selection . . . . .            | 413        |
| 22.7: 4-Channel “no hole” PI . . . . .           | 413        |
| 22.8: PWM Ground Balance. . . . .                | 414        |
| 22.9: Digital Design . . . . .                   | 416        |
| 22.10: Direct Sampling. . . . .                  | 416        |
| 22.11: Split Coil . . . . .                      | 417        |
| <b>Chapter 23: Bipolar PI . . . . .</b>          | <b>419</b> |
| Transmitter . . . . .                            | 420        |
| 23.1: H-Bridge Design . . . . .                  | 421        |
| 23.2: Differential Coil Design . . . . .         | 424        |
| Receiver . . . . .                               | 426        |
| 23.3: Demods & GB . . . . .                      | 426        |
| 23.4: Audio Stage . . . . .                      | 428        |
| Design: Bipolar PI (Pulse-5) . . . . .           | 429        |
| Explore . . . . .                                | 434        |
| 23.5: Differential Dual Coil Variants . . . . .  | 434        |
| 23.6: Simultaneous Differential Pulsing. . . . . | 434        |
| 23.7: TDI Audio . . . . .                        | 434        |
| 23.8: Security Walk-Through . . . . .            | 435        |

## Part 6: Advanced Methods

|   |            |
|---|------------|
| <b>Chapter 24: Multifrequency . . . . .</b>         | <b>441</b> |
| 24.1: Overview . . . . .                            | 441        |
| 24.2: Case Studies. . . . .                         | 443        |
| 24.2.1: Fisher CZ . . . . .                         | 443        |
| 24.2.2: White’s DFX . . . . .                       | 444        |
| 24.2.3: Minelab BBS/FBS . . . . .                   | 445        |
| 24.2.4: White’s V3 . . . . .                        | 446        |
| 24.2.5: Minelab Equinox . . . . .                   | 447        |
| 24.2.6: Boosted Sequential Multifrequency . . . . . | 448        |
| 24.3: Multifrequency Signals . . . . .              | 449        |
| 24.3.1: Measuring MF Target Responses . . . . .     | 449        |
| 24.3.2: Ground Response . . . . .                   | 450        |

|                                     |            |
|-------------------------------------|------------|
| 24.3.3: Salt                        | 450        |
| 24.3.4: Iron Responses              | 450        |
| 24.3.5: Eddy Responses              | 451        |
| 24.4: Multifrequency Processing     | 452        |
| 24.4.1: Correlated Processing       | 452        |
| 24.4.2: Composite Processing        | 453        |
| 24.4.3: Salt Notching               | 454        |
| 24.5: Multifrequency Efficiency     | 455        |
| 24.6: Multifrequency Design         | 456        |
| 24.6.1: Transmitter                 | 456        |
| 24.6.2: Preamp                      | 457        |
| 24.6.3: Channel Filters             | 457        |
| 24.6.4: Demods                      | 457        |
| 24.6.5: Remainder                   | 458        |
| Explore                             | 458        |
| 24.7: Narrowband Demodulators       | 458        |
| 24.8: Asynchronous Demodulation     | 458        |
| 24.9: Dual Preamps                  | 458        |
| 24.10: Moreland-Kelley Filter       | 459        |
| <b>Chapter 25: Advanced PI</b>      | <b>461</b> |
| Multi-Period PI                     | 461        |
| 25.1: Proportional Timing           | 461        |
| 25.2: Multi-Voltage Drive           | 462        |
| 25.3: Equalized Multi-Voltage Drive | 463        |
| 25.4: Multi-Step Drive              | 465        |
| 25.5: Two-Slope Ground Balance      | 466        |
| 25.6: Noise                         | 467        |
| Constant-Current PI                 | 468        |
| 25.7: Brute-Force Drive             | 469        |
| 25.8: Recycling Kickstart Methods   | 469        |
| 25.9: Square Wave Drive             | 470        |
| 25.10: Current Control              | 472        |
| 25.11: Switching Losses             | 472        |
| Explore                             | 474        |
| 25.12: Flyback Isolation            | 474        |
| 25.13: Dynamic Damping              | 475        |
| 25.14: Iron Discrimination          | 476        |
| <b>Chapter 26: Hybrid Methods</b>   | <b>477</b> |
| Half-Sine                           | 477        |
| 26.1: Transmitter                   | 477        |
| 26.2: Hybrid Response               | 478        |
| 26.3: Efficiency                    | 479        |
| 26.4: Slew Rate                     | 479        |
| 26.5: Ideal Target Responses        | 480        |
| 26.6: Actual Target Responses       | 481        |
| 26.7: Receiver                      | 482        |
| 26.8: Conceptual Circuit            | 482        |
| 26.9: Processing                    | 483        |
| Truncated Half-Sine                 | 484        |
| 26.10: Transmitter                  | 484        |
| 26.11: Receiver                     | 485        |
| Other Hybrids                       | 486        |
| 26.12: PI-TX Response               | 486        |
| 26.13: Gold Sweeper                 | 487        |

|   |     |
|---|-----|
| 26.14: Pulse Devil . . . . .              | 487 |
| 26.15: Voodoo . . . . .                   | 488 |
| Explore . . . . .                         | 489 |
| 26.16: Multifrequency Half-Sine . . . . . | 489 |
| 26.17: Faking a Hybrid . . . . .          | 490 |

## Part 7: Leftovers

|  |     |
|--|-----|
| <b>Chapter 27: Oddball Circuits</b> . . . . .              | 493 |
| 27.1: Thomas Scarborough . . . . .                         | 493 |
| 27.1.1: Beat Balance . . . . .                             | 493 |
| 27.1.2: CCO Metal Detector . . . . .                       | 493 |
| 27.2: Balanced Inductor Design . . . . .                   | 494 |
| 27.3: Minelab Go Find . . . . .                            | 495 |
| 27.4: Buckless Concentric Coil . . . . .                   | 495 |
| 27.5: White's Mono-Coil TR . . . . .                       | 496 |
| 27.6: Tarsacci . . . . .                                   | 496 |
| 27.7: Inductive Sensor Chips . . . . .                     | 496 |
| 27.7.1: CS209A . . . . .                                   | 496 |
| 27.7.2: LDC1000 . . . . .                                  | 497 |
| <b>Chapter 28: Things &amp; Stuff &amp; Junk</b> . . . . . | 499 |
| 28.1: Is it an antenna? . . . . .                          | 499 |
| 28.2: Transmit Power . . . . .                             | 499 |
| 28.3: FCC Regulations . . . . .                            | 500 |
| 28.4: Power Limits . . . . .                               | 502 |
| 28.5: Metal in the Coil . . . . .                          | 502 |
| 28.6: Power Line Interference . . . . .                    | 503 |
| 28.7: Detector Cross-Talk Interference . . . . .           | 504 |
| 28.8: Silent EMI . . . . .                                 | 504 |
| 28.9: The Halo Effect, Part 1 . . . . .                    | 504 |
| 28.10: The Halo Effect, Part 2 . . . . .                   | 505 |
| 28.11: Treasure Hunting Methods . . . . .                  | 505 |
| 28.12: Treasure Hunting Mythology . . . . .                | 506 |
| 28.13: Great Ideas . . . . .                               | 507 |
| 28.14: Going Solo . . . . .                                | 507 |
| 28.15: Counterfeiting . . . . .                            | 508 |

## Part 8: Appendices

|  |     |
|--|-----|
| <b>Chapter A: Magnetic Field Probe</b> . . . . . | 513 |
| A.1: Theory . . . . .                            | 513 |
| A.2: Sensor . . . . .                            | 514 |
| A.3: Remaining Design . . . . .                  | 515 |
| A.4: Construction . . . . .                      | 518 |
| A.5: Calibration . . . . .                       | 518 |
| A.6: Usage . . . . .                             | 520 |
| <b>Chapter B: Coil Calculations</b> . . . . .    | 523 |
| B.1: Solenoidal Coils . . . . .                  | 523 |
| B.2: Short Coils . . . . .                       | 524 |
| B.3: General Short/Long Coils . . . . .          | 524 |
| B.4: Spiral Inductors . . . . .                  | 525 |
| B.5: Accuracy . . . . .                          | 525 |
| B.6: Coil Calculator . . . . .                   | 525 |
| B.7: Non-Circular Coils . . . . .                | 526 |
| <b>Chapter C: PI Math</b> . . . . .              | 527 |
| The Transmit Side . . . . .                      | 527 |

|  |     |
|--|-----|
| C.1: TX Turn-On Response .....                   | 527 |
| C.2: TX Turn-Off Response .....                  | 529 |
| The Target Side .....                            | 533 |
| C.3: TX Turn-On Eddies .....                     | 533 |
| C.4: TX Turn-Off Eddies .....                    | 536 |
| C.5: Complete Eddy Response .....                | 537 |
| C.6: Target Response vs Turn-Off Slew Rate ..... | 539 |
| The Receive Side .....                           | 540 |
| C.7: RX Coil Response .....                      | 540 |
| C.8: Sampling Integrator .....                   | 542 |
| C.9: EFE Sample .....                            | 543 |
| C.10: Ground Balance .....                       | 544 |
| C.11: Power Consumption .....                    | 546 |
| <b>Chapter D: Resources</b> .....                | 547 |
| Web Sites .....                                  | 547 |
| Books .....                                      | 548 |
| Research Papers .....                            | 548 |
| Periodical Articles .....                        | 550 |
| Other .....                                      | 556 |
| <b>Chapter E: Patents</b> .....                  | 557 |
| E.1: The Patent Minefield .....                  | 557 |
| E.2: Patent Requirements .....                   | 558 |
| Patents .....                                    | 559 |
| E.3: Proximity Methods .....                     | 559 |
| E.4: Induction Balance (TR/VLF) Methods .....    | 560 |
| E.5: Multifrequency .....                        | 562 |
| E.6: Pulse Induction/Time Domain .....           | 563 |
| E.7: Hybrid/Other Methods .....                  | 565 |
| E.8: Coils .....                                 | 565 |
| E.9: Eddy techniques .....                       | 566 |
| E.10: DSP Methods .....                          | 567 |
| E.11: Security .....                             | 567 |
| E.12: Mine Detection .....                       | 567 |
| E.13: Misc. ....                                 | 568 |
| E.14: Pre-1970 .....                             | 569 |
| <b>Chapter F: Glossary</b> .....                 | 571 |
| <b>Index</b> .....                               | 575 |